

Pre-lab Report 3

ECE 218- L01


Dr. Borkar

Lab Instructor: Muyu Yang

Alan Biju Palayil

Lab Date: 02/15/2021

Preliminary Assignment

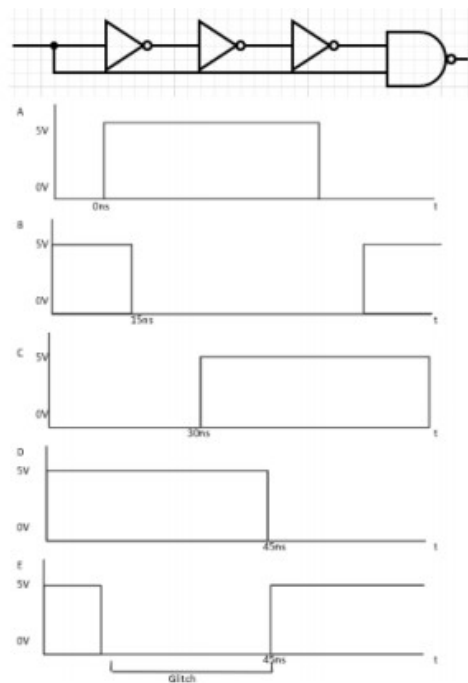


1.


A	B	C	$(AB)'$	$(BC)'$	$(AC)'$	Output	Red	Green
LOW	LOW	LOW	HIGH	HIGH	HIGH	LOW	LIT	OFF
LOW	LOW	HIGH	HIGH	HIGH	HIGH	LOW	LIT	OFF
LOW	HIGH	LOW	HIGH	HIGH	HIGH	LOW	LIT	OFF
LOW	HIGH	HIGH	HIGH	LOW	HIGH	HIGH	OFF	LIT
HIGH	LOW	LOW	HIGH	HIGH	HIGH	LOW	LIT	OFF
HIGH	LOW	HIGH	HIGH	HIGH	LOW	HIGH	OFF	LIT
HIGH	HIGH	LOW	LOW	HIGH	HIGH	HIGH	OFF	LIT
HIGH	HIGH	HIGH	LOW	LOW	LOW	HIGH	OFF	LIT

2.

Schematics

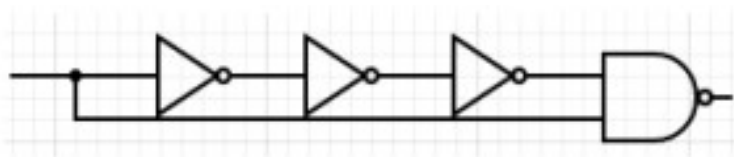

Breadboard Layout

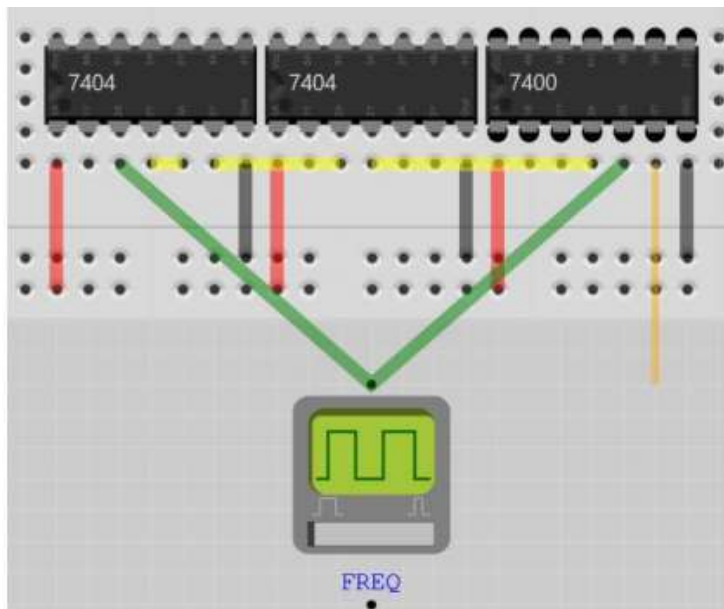

Data Table

Majority circuit

Switch 1	Switch 2	Switch 3	LED
Open	Open	Open	
Open	Open	Closed	
Open	Closed	Open	
Open	Closed	Closed	
Closed	Open	Open	
Closed	Open	Closed	
Closed	Closed	Open	
Closed	Closed	Closed	