

## Pre-Lab 7

ECE218-L01

Dr. Borkar

TA: Muyu Yang


Alan Palayil

Lab Date: 12 Apr 21

Due Date: 12 Apr 21

### Preliminary Questions:

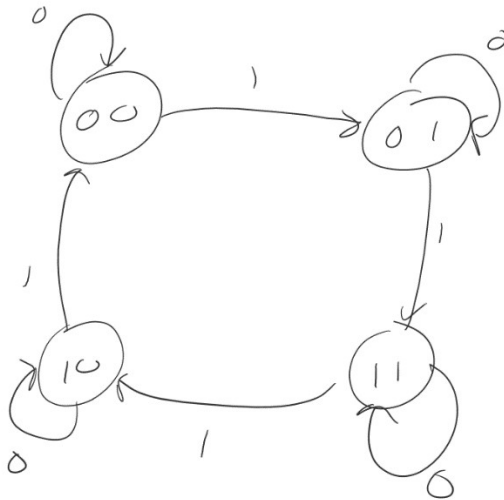1. A 10-bit binary counter goes through 1024 different states.
- 2.



Present State		Next State (AB)	
a	b	EN=0	EN=1
0	0	00	01
0	1	01	11
1	1	11	10
1	0	10	00

3.

EN\ab	00	01	11	10
0	0	0	1	1
1	0	1	1	0


$$A = ENb + EN'a$$

EN\ab	00	01	11	10
0	0	1	1	0
1	1	1	0	0


$$B = EN'b + ENa'$$

See schematic


4.

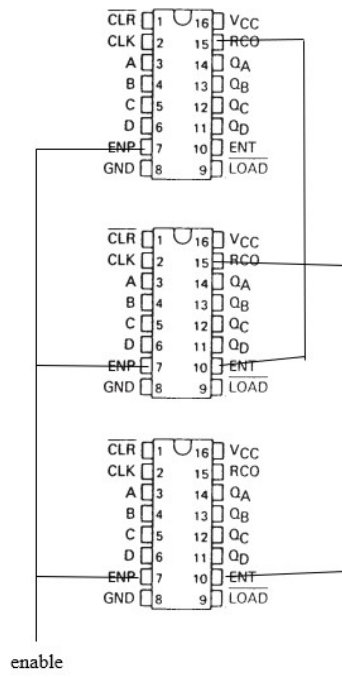


5.

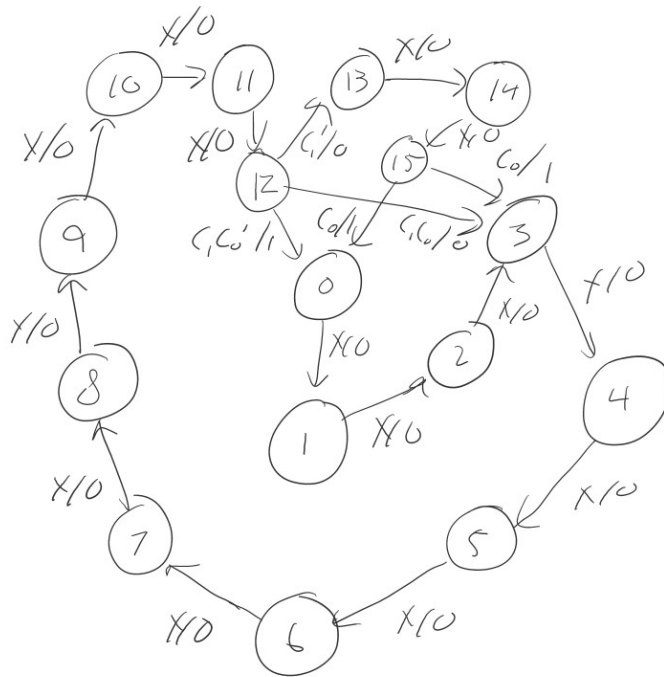

## Schematics

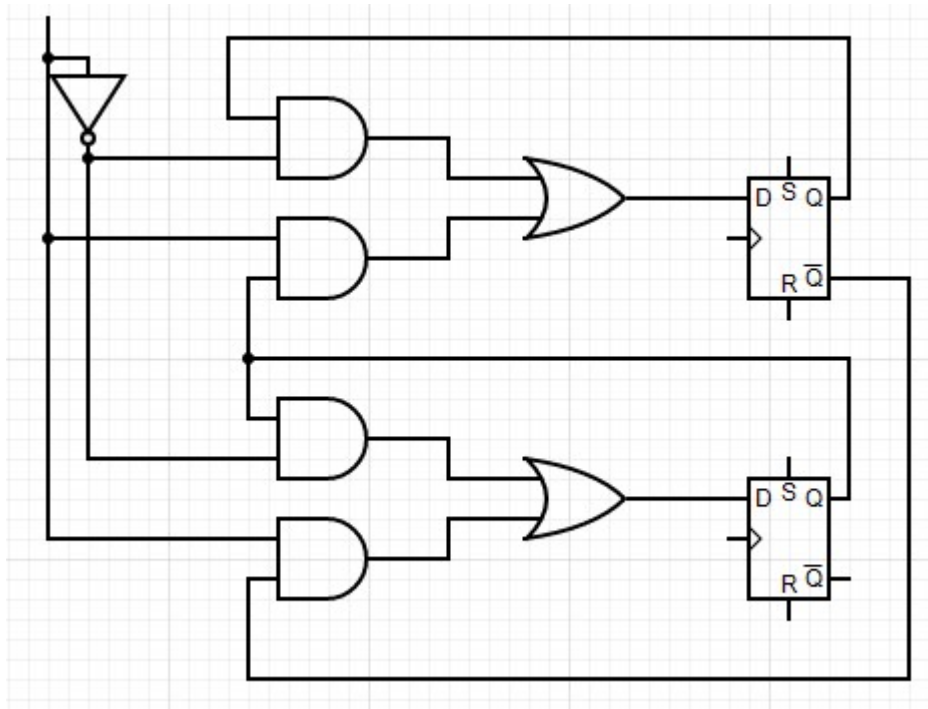


2-Bit Gray Code Counter

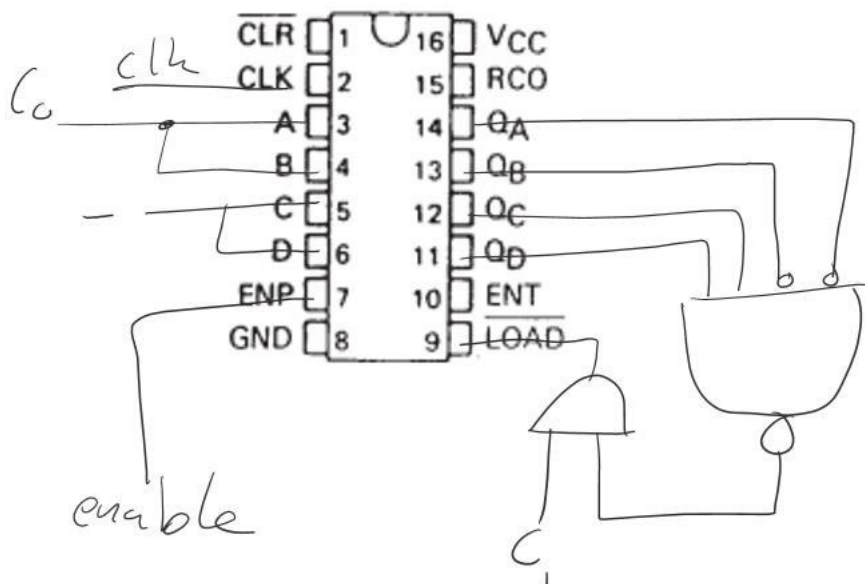


Specialized Counter

## Breadboards

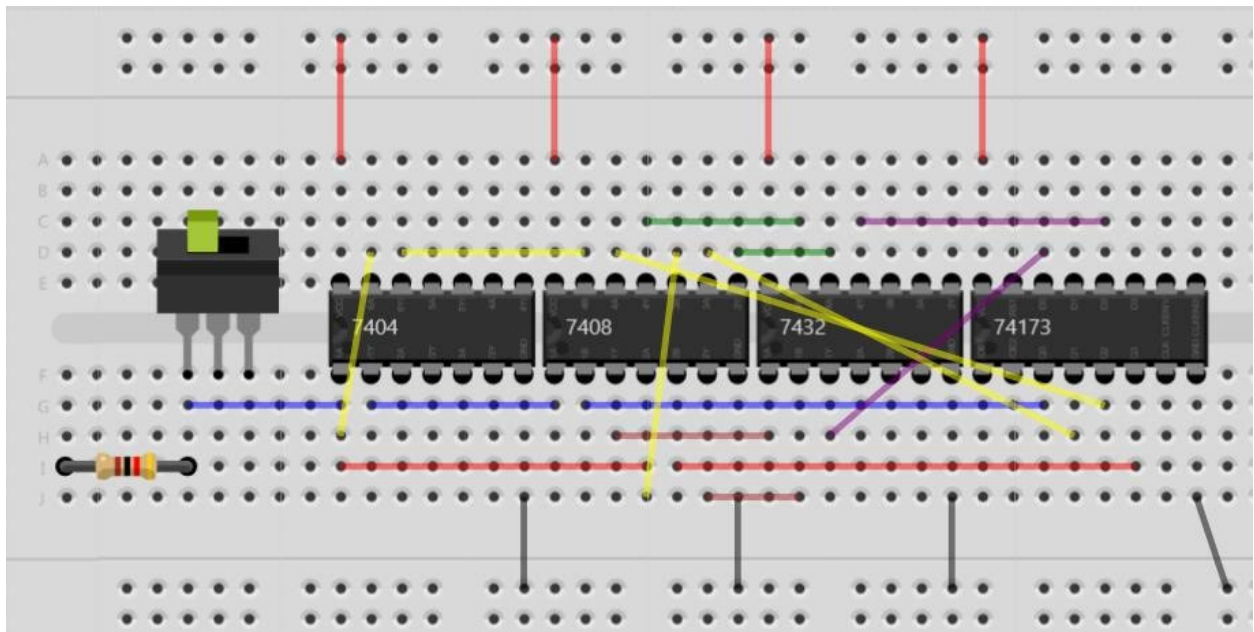

## 2-Bit Gray Code Counter

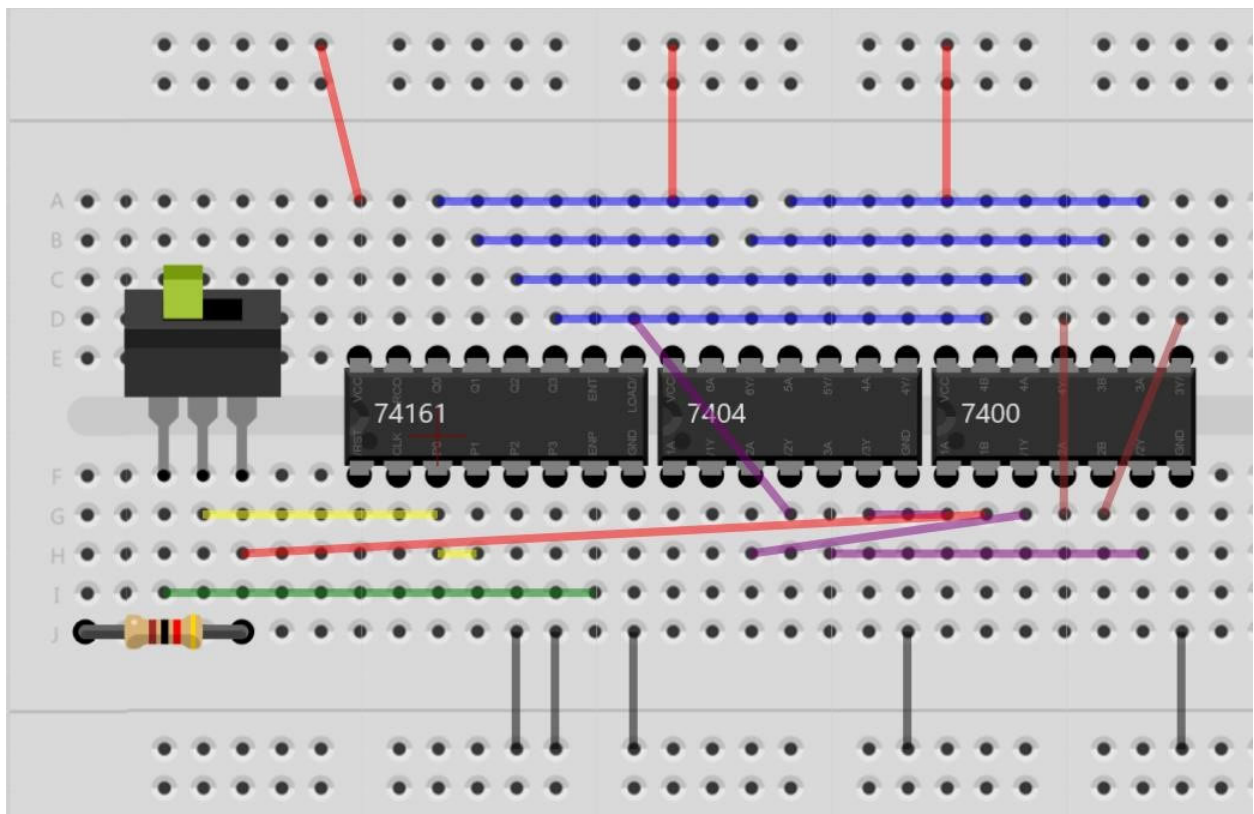

### Specialized Counter

## Data Sheet

### 2-bit Gray Code Counter

Input	Output

C <sub>0</sub>	C <sub>1</sub>	Input	Output
0	0		
0	1		
1	0		
1	1		